

5.40 The inverting amplifier in the circuit in Fig. P5.40 has an input resistance of $400\text{ k}\Omega$, an output resistance of $2\text{ k}\Omega$, and an open-loop gain of $500,000$. Assume that the amplifier is operating in its linear region.

- Calculate the voltage gain (v_o/v_g) of the amplifier.
- Calculate the value of v_n in microvolts when $v_g = 50\text{ mV}$.
- Calculate the resistance seen by the signal source (v_g).
- Repeat (a)–(c) using the ideal model for the op amp.


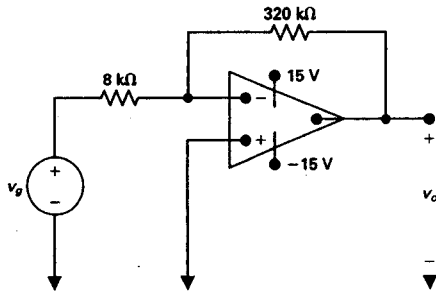


Figure P5.40

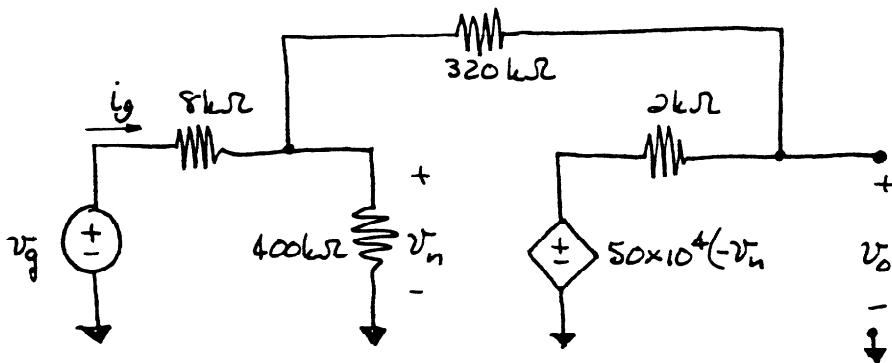

$$\frac{v_n}{400} + \frac{v_n - v_g}{8} + \frac{v_n - v_o}{320} = 0$$

$$\therefore 41.8v_n - v_o = 40v_g$$

$$\frac{v_o - 500,000(-v_n)}{2} + \frac{v_o - v_n}{320} = 0$$

$$\therefore 80 \times 10^6 v_n + 161v_o = 0$$

$$\Delta = \begin{vmatrix} 41.8 & -1 \\ 80 \times 10^6 & 161 \end{vmatrix} = 80,006,729.8$$

$$N_o = \begin{vmatrix} 41.8 & 40v_g \\ 80 \times 10^6 & 0 \end{vmatrix} = -32 \times 10^8 v_g$$

$$v_o = \frac{N_o}{\Delta} = -39.997v_g; \quad \text{so } \frac{v_o}{v_g} = -39.997$$

$$[b] \quad N_1 = \begin{vmatrix} 40v_g & -1 \\ 0 & 161 \end{vmatrix} = 6440v_g$$

$$v_n = \frac{N_1}{\Delta} = 8.05 \times 10^{-5}v_g$$

$$v_g = 50 \text{ mV}, \quad v_n = 4.02 \mu \text{ V}$$

$$[c] \quad i_g = \frac{v_g - v_n}{8} = \frac{v_g - 8.05 \times 10^{-5}v_g}{8}$$

$$R_g = \frac{v_g}{i_g} = \frac{v_g}{v_g - 8.05 \times 10^{-5}v_g} \cdot (8000) = 8000.644 \Omega$$

$$[d] \quad \frac{v_o}{v_g} = -40; \quad v_n = 0 \text{ V}; \quad R_g = 8000 \Omega$$