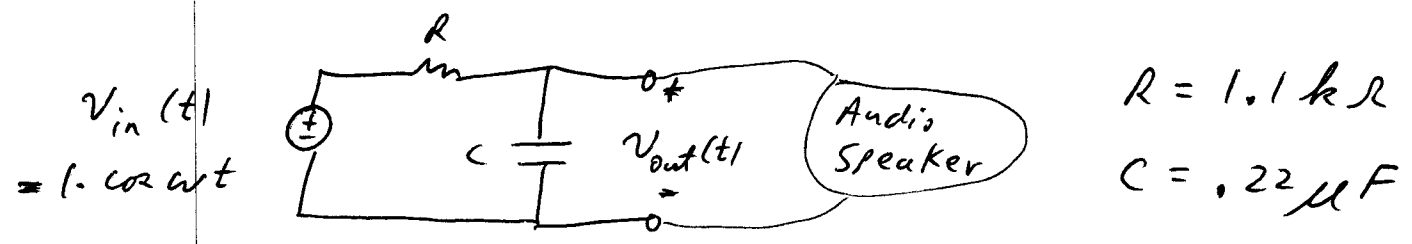


Sinusoidal Response of Circuits

(Frequency selective "filters")

Relevant reading in the text:

Class demonstration to motivate "filters":



Vary ω , the frequency of input sine wave.

Low frequencies: (Below $f = 658 \text{ Hz}$)

V_{out} is about the same size as V_{in} , and tone is audible.

High frequencies: (Above $f = 658 \text{ Hz}$)

V_{out} is smaller than V_{in} , and tone is less loud.

Our goal is to understand what is happening in this circuit.

Such "filters" are used in many applications: Tune radios, TVs, treble + bass on stereo, equalizers, Dolby for cassettes, compact discs,...

Basic idea: Circuit is a voltage divider.

The capacitor "impedance" decreases as ω increases, so V_{out} gets smaller as ω increases.

Outline:

- we have reviewed sine waves on a separate set of notes.
- we will define "phasors", which describe sine waves by a complex number.
- we will review the arithmetic of complex numbers
- we will define "impedance", which is like a resistance that varies with frequency.
- we will apply phasors + impedance to circuits.

Phasors:

A phasor characterizes the amplitude + phase of a sinusoidal time signal:

Time signal: $v(t) = A \cos[\omega t + \phi]$

Phasor: $\underline{v} = A \angle \phi = A e^{j\phi}$

Re Frequency ω is omitted from the phasor.

Re rationale is that "linear" circuits (the kind we've been studying) do not change the frequency ω - they only change the amplitude + phase of a sine wave.

[Recall the RC demo on p. 1; the output has the same frequency as the input, but it can be smaller in amplitude + shifted in phase.]

Examples:

<u>Time Signal</u>	<u>Phasor</u>
$v(t) = 10.1 \cos(100t)$	$\underline{v} =$
$v(t) = 2 \cos(5t + 30^\circ)$	$\underline{v} =$
$v(t) = \cos(77t)$	$\underline{v} = 4 \angle -35^\circ$

We manipulate phasors as complex numbers.

Recall "imaginary" numbers: $j = \sqrt{-1}$

(You may have used $i = \sqrt{-1}$ in math - we use j since i is used for current)

Imaginary numbers arise in solving equations like $x^2 = -4 \Rightarrow x = j2$


Because: $(j2)^2 = j^2 \cdot 2^2 = (\sqrt{-1})^2 \cdot 4 = -4$

So $j^2 = -1 \Rightarrow$ remember that.

"Complex" numbers have a real part and an imaginary part.

Ex: $3 + j4$

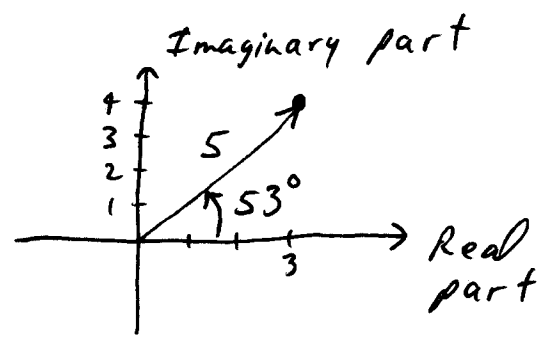We can visualize this as a vector in the "complex plane":




$3 + j4$ is the "rectangular form".

An equivalent representation is the "polar form":

$5 \angle 53^\circ$ = vector of length 5 at angle 53° with real axis.


How I got this:

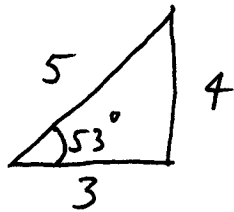

$$5 = \sqrt{3^2 + 4^2} = \sqrt{9 + 16}$$

$$53^\circ = \tan^{-1} \frac{4}{3}$$

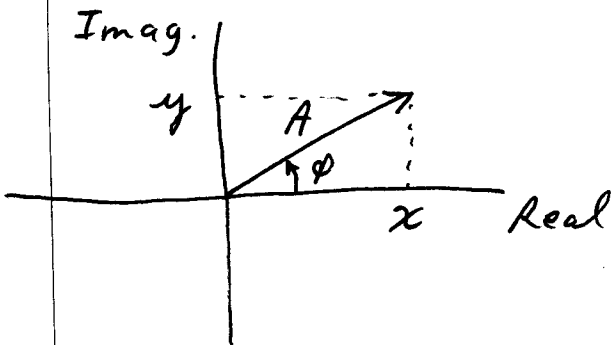General conversion between rectangular + polar forms:



$$x + jy = A \angle \phi$$

If know $x + jy$:

$$A = \sqrt{x^2 + y^2} = \text{"magnitude"}$$

$$\phi = \tan^{-1} \frac{y}{x} \left\{ \begin{array}{l} \text{Need to be} \\ \text{careful about} \\ \text{quadrant} \end{array} \right.$$

If know $A \angle \phi$:

$$x = A \cos \phi$$

$$y = A \sin \phi$$

A phasor $A \angle \phi$ is like a vector, with one additional feature: phasors can be multiplied in a way vectors cannot.

Complex number arithmetic:

Addition + subtraction: Operate on real + imaginary parts separately.

$$(3 + j4) + (-1 + j2) = (3-1) + j(4+2)$$

$$= 2 + j6$$

Use rectangular form to add/subtract.

Multiplication: with rectangular form, use algebra, & remember $j^2 = -1$:

$$(3 + j4) \cdot (-1 + j2) = (3)(-1) + (3)(j2) + (j4)(-1)$$

$$+ (j4)(j2)$$

$$= -3 + j6 + j(-4) + j^2(8)$$


$$= -3 - 8 + j(6-4) = -11 + j2$$

Multiplication + Division are simpler with polar form:

$$(A_1 \angle \phi_1) \cdot (A_2 \angle \phi_2) = A_1 \cdot A_2 \angle (\phi_1 + \phi_2)$$

$$\frac{A_1 \angle \phi_1}{A_2 \angle \phi_2} = \frac{A_1}{A_2} \angle (\phi_1 - \phi_2)$$

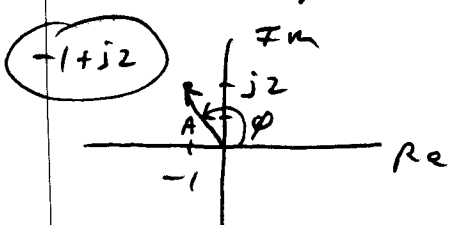For example above: $3 + j4 = 5 \angle 53^\circ$



$$A = \sqrt{1^2 + 2^2} = \sqrt{5}$$

$$\phi = 180^\circ - \tan^{-1} \frac{2}{1} = 110^\circ$$



(6)


$$\begin{aligned}
 (3+j4) \cdot (-1+j2) &= (5 \angle 53^\circ) \cdot (\sqrt{5} \angle 110^\circ) \\
 &= 5 \cdot \sqrt{5} \angle 170^\circ \\
 &= 5 \cdot \sqrt{5} \cos 170^\circ + j 5 \sqrt{5} \sin 170^\circ \\
 &= -11 + j2, \text{ which agrees.}
 \end{aligned}$$

Your calculator may do complex number arithmetic — feel free to use those capabilities.

So we will think of phasors as complex numbers, and manipulate them as complex numbers.

Time Function: $v(t) = A \cos(\omega t + \phi)$

Phasor: $\underline{v} = A \angle \phi$

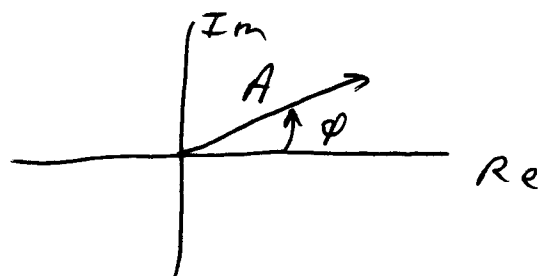

This simplifies the analysis — it is easier than solving differential eqs.!

Impedance


Recall Ohm's law for resistors:

$$R = \frac{v(t)}{i(t)}$$


The current + voltage are always related this way for a resistor, even if the voltage + current varies with time. (For example, $v(t) = 2 \cos(100t)$.)

We want to get a similar relation for a capacitor. We will take the ratio of voltage + current phasors.

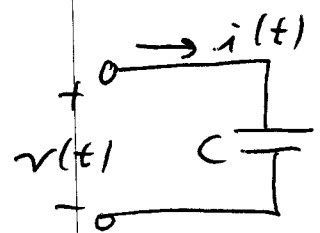Consider $v(t) = A \cos \omega t$ across cap.:


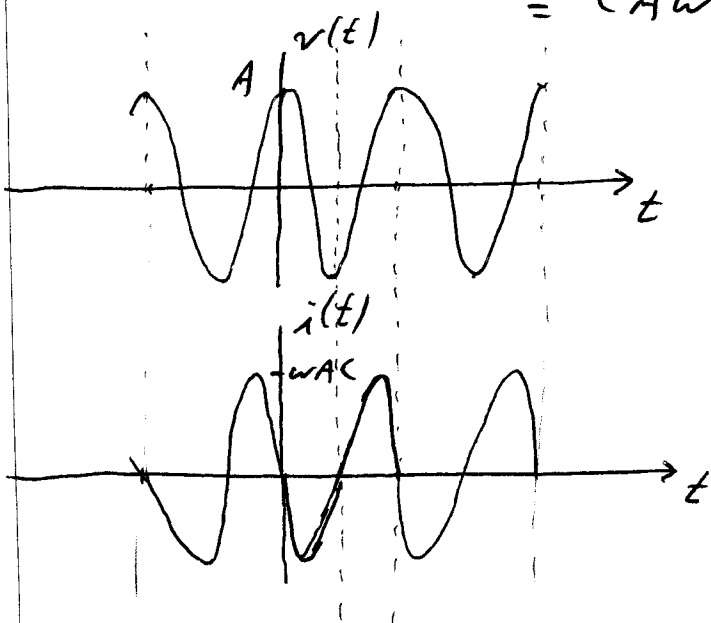
$$\begin{aligned}
 i(t) &= C \frac{dv}{dt} \\
 &= C \cdot \frac{d}{dt} A \cos \omega t \\
 &= -CA \omega \sin \omega t \\
 &= CA \omega \cos[\omega t + 90^\circ]
 \end{aligned}$$



Current is scaled in amplitude by factor ωC , and shifted in phase by 90° , relative to voltage.



Phasors for voltage + current:

$$v(t) = A \cos \omega t$$

$$i(t) = CA\omega \cos[\omega t + 90^\circ]$$

$$\underline{v} = A \angle 0^\circ$$
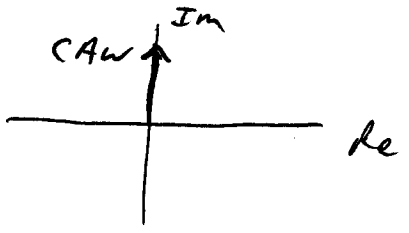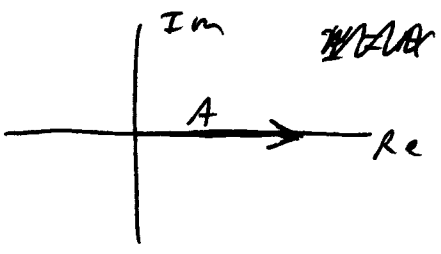
$$\underline{i} = CA\omega \angle 90^\circ$$



$$\underline{v} = A$$

$$\underline{i} = j(CA\omega)$$

Note the phasors \underline{v} and \underline{i} convey the amplitude + phase difference between voltage + current.


Define impedance of capacitor:

$$Z_c = \frac{\underline{v}}{\underline{i}} = \frac{A}{jCA\omega} = \boxed{\frac{1}{j\omega C}}$$

- This is like a resistance: it relates voltage + current flow, like Ohm's law.
- Note the impedance varies with freq. ω . In fact, it gets smaller as ω increases, which agrees with the demo. on page 1.
- The impedance is a complex number, which allows it to account for the phase shift between $v(t)$ and $i(t)$.

Ohm's Law for phasors + impedance:
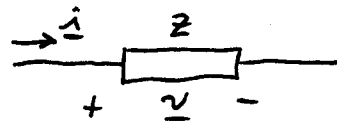
$$\underline{v} = \underline{i} \underline{Z}$$




Here v , i , and Z are complex numbers.


Impedance of resistors, capacitors, inductors:

General Formulas

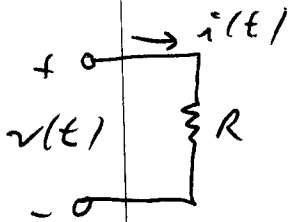
Phasors + impedance for sinusoidal signals



$$v(t) = R i(t)$$

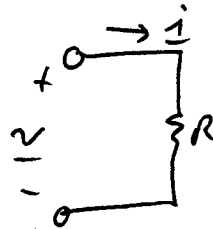


$$\underline{v} = R \underline{i}$$

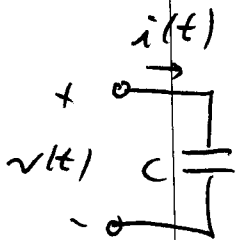


$$i(t) = C \frac{dv}{dt}$$
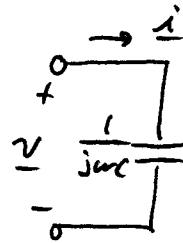
$$v(t) = \frac{1}{C} \int_{-\infty}^t i(x) dx$$



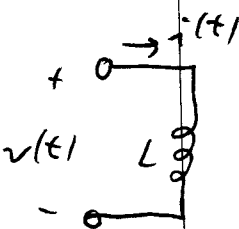
$$\underline{v} = \left(\frac{1}{j\omega C} \right) \underline{i}$$




$$v(t) = L \frac{di}{dt}$$
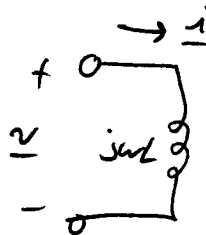
$$i(t) = \frac{1}{L} \int_{-\infty}^t v(x) dx$$




$$\underline{v} = (j\omega L) \underline{i}$$

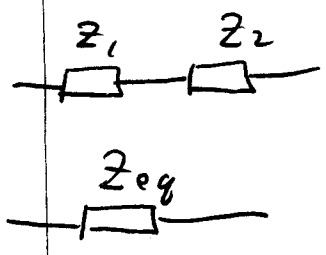- Can transform circuit elements to impedances
- Impedances in series/parallel combine like resistors






$$Z_{eq} = Z_1 + Z_2$$

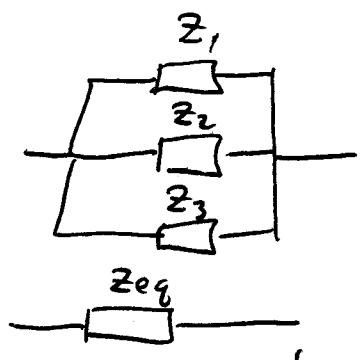

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

Examples:

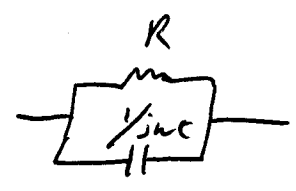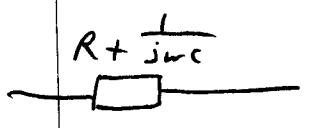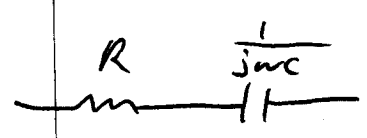

$$\frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{j\omega RC + 1}$$


The actual impedance will depend on the values of R, C, and the frequency ω of the applied sine wave.

The impedance changes with Freq. ω .


All of our circuit analysis tools apply to circuits with impedances + phasors:

- Generalized Ohm's Law: $\underline{v} = \underline{i} \underline{Z}$
 - KVL, KCL
 - Voltage divider
 - Nodal + mesh analysis
 -
- Thevenin
 Superposition
 Op amps
 ...

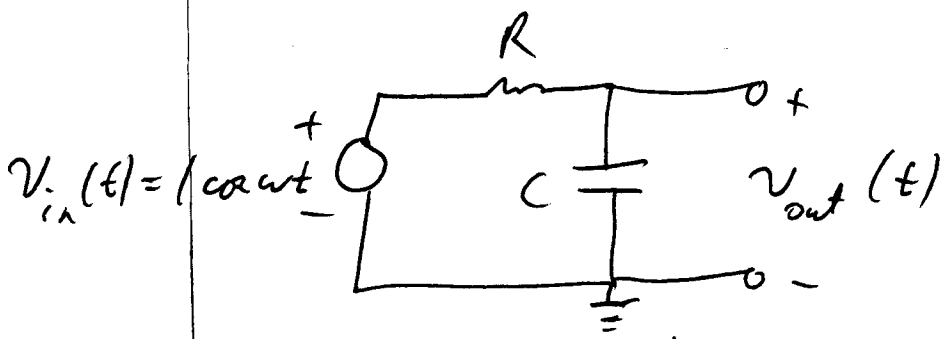Now we can understand the RC circuit on page 1:



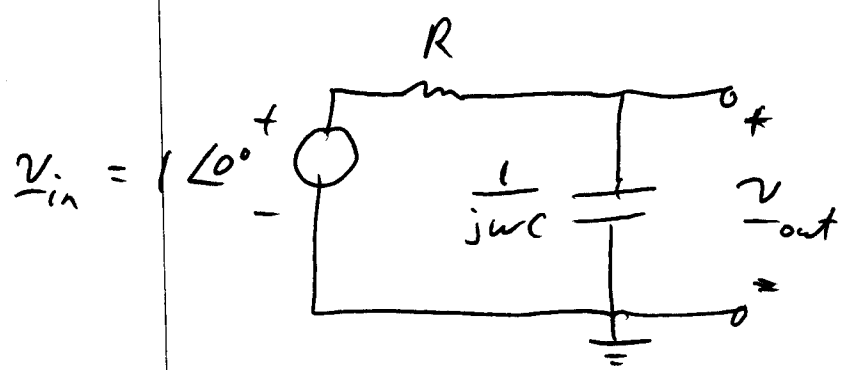Redraw circuit with phasors & impedances - we will then be able to solve for the output voltage phasor, for a given input freq. ω .



Treat impedances like resistors:

$\underline{V}_{out} =$