

## Homework 12 Answers

Please be sure to clearly show your work in the solutions that you submit. Your approach is much more important than obtaining the correct numerical answer.

**Problem 7.23:** Hint: Use the identity  $A\cos(\omega t + \theta) = A[\cos\omega t \cos\theta - \sin\omega t \sin\theta]$

**Problem 7.25:**  $9.4 \cos(2\pi \times 10^4 t - 21.48^\circ)$  (mA)

**Problem 7.27:** (a)  $(2.7 - j18.5) \Omega$ . (c)  $(69.2 - j64.4) \Omega$  (e)  $(12.67 - j10.98) \Omega$ .

**Problem 7.31:**  $(2 + j3.46) \text{ k}\Omega$ .

**Problem 7.34 (optional problem):** Two answers are possible, and both are between 150 and 350 rad/sec (exact answer is not given here).

**Problem 7.35:**  $V_{Th} = 116.5 \angle -22.5^\circ \text{ V}$ ,  $Z_{Th} = (50 - j43.25) \Omega$ . Note for part (c), you should draw the Thevenin equivalent with a sinusoidal voltage source in series with a R and C (why a C and not L?), and you should specify values for R and C.

**Problem 7.37:**  $V_{Th} = -12 \text{ V}$ , value of  $Z_{Th}$  is not given here.

**Problem 7.47:**  $i_C(t) = 1.25 \cos(400t - 6.352^\circ)$  (A).

**Problem 7.48:** You should find the node voltage phasors, but the final answer should be enough for you to check your work:  $I_C = 17.334$  (A).

**Problem 7.51 & 7.52:**  $1.93 \angle 4.9^\circ \text{ A}$

**Problem 7.56:**  $1.8 \cos(2.5 \times 10^4 t + 53.13^\circ)$  (A).