

## Homework 6 Answers

Please be sure to clearly show your work in the solutions that you submit. Your approach is much more important than obtaining the correct numerical answer.

**Problem 3.58:**  $V_{Th} = 17.5 \text{ V}$ ,  $R_{Th} = 4.5 \ \Omega$  (be sure to show the *polarity* of the voltage source in your Thevenin equivalent circuit)

**Problem 3.59:**  $I_N = 7.7 \text{ A}$ ,  $R_{Th} = 4.5 \ \Omega$  (be sure to show the *direction* of the current source in your Norton equivalent circuit)

**Supplemental Problem:** (b)  $v_L = 1.55 \text{ V}$