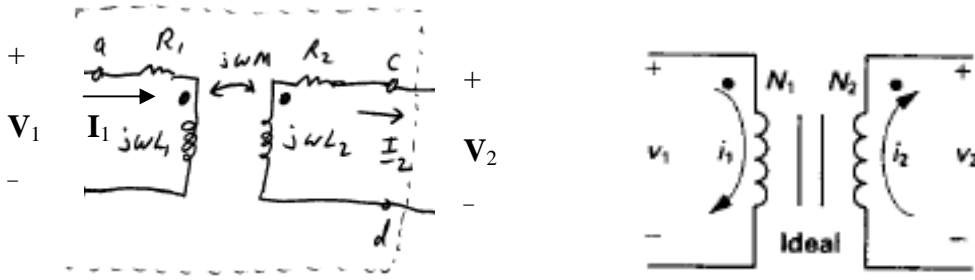


Linear Transformer → Ideal Transformer



Consider linear and ideal transformers attached to Circuit 1 and Circuit 2.

$$\begin{aligned} \mathbf{V}_1 &= (R_1 + j\omega L_1)\mathbf{I}_1 - j\omega M\mathbf{I}_2 & ? \rightarrow ? & \frac{\mathbf{V}_1}{N_1} = \frac{\mathbf{V}_2}{N_2} \\ -\mathbf{V}_2 &= -j\omega M\mathbf{I}_1 + (R_2 + j\omega L_2)\mathbf{I}_2 & & N_1\mathbf{I}_1 = N_2\mathbf{I}_2 \end{aligned}$$

$$L_1 = N_1^2 \mathcal{P}_{12} \left( 1 + \frac{\mathcal{P}_{11}}{\mathcal{P}_{12}} \right) = N_1^2 \mathcal{P}_{12} g_1, \quad g_1 \geq 1, \quad L_2 = N_2^2 \mathcal{P}_{12} \left( 1 + \frac{\mathcal{P}_{22}}{\mathcal{P}_{12}} \right) = N_2^2 \mathcal{P}_{12} g_2, \quad g_2 \geq 1$$

$$M = N_1 N_2 \mathcal{P}_{12} \quad \frac{M^2}{L_1 L_2} = k^2 = \frac{1}{g_1 g_2} \leq 1$$

Perfect coupling :  $k^2 = 1 \Rightarrow g_1 = g_2 = 1$

Substitute in linear transformer equations for  $L_1, L_2, M$  :

$$\mathbf{V}_1 = (R_1 + j\omega N_1^2 \mathcal{P}_{12} g_1)\mathbf{I}_1 - (j\omega N_1 N_2 \mathcal{P}_{12})\mathbf{I}_2 \Rightarrow \left( \frac{N_2}{N_1} \right) \mathbf{V}_1 = \left( \frac{N_2}{N_1} R_1 + j\omega N_1 N_2 \mathcal{P}_{12} g_1 \right) \mathbf{I}_1 - (j\omega N_2^2 \mathcal{P}_{12}) \mathbf{I}_2 \rightarrow \mathbf{V}_2$$

$$\mathbf{V}_2 = (j\omega N_1 N_2 \mathcal{P}_{12})\mathbf{I}_1 - (R_2 + j\omega N_2^2 \mathcal{P}_{12} g_2)\mathbf{I}_2 \Rightarrow \left( \frac{N_1}{N_2} \right) \mathbf{V}_2 = (j\omega N_1^2 \mathcal{P}_{12}) \mathbf{I}_1 - \left( \frac{N_1}{N_2} R_2 + j\omega N_1 N_2 \mathcal{P}_{12} g_2 \right) \mathbf{I}_2 \rightarrow \mathbf{V}_1$$

What must occur to achieve the limits on the right side?

$$\left[ \omega N_1 N_2 \mathcal{P}_{12} g_1 \gg \frac{N_2}{N_1} R_1 \text{ or } \omega L_1 \gg R_1 \right] \text{ and } \left[ \omega N_1 N_2 \mathcal{P}_{12} g_2 \gg \frac{N_1}{N_2} R_2 \text{ or } \omega L_2 \gg R_2 \right] \text{ and } [g_1 = g_2 = 1]$$

Now solve the linear transformer equations for the currents:

$$\mathbf{I}_1 = \frac{\mathbf{V}_1}{R_1 + j\omega N_1^2 \mathcal{P}_{12} g_1} + \frac{j\omega N_1 N_2 \mathcal{P}_{12}}{R_1 + j\omega N_1^2 \mathcal{P}_{12} g_1} \mathbf{I}_2 \Rightarrow \frac{N_1}{N_2} \mathbf{I}_1 = \frac{\frac{N_1}{N_2} \mathbf{V}_1}{R_1 + j\omega N_1^2 \mathcal{P}_{12} g_1} + \frac{j\omega N_1^2 \mathcal{P}_{12}}{R_1 + j\omega N_1^2 \mathcal{P}_{12} g_1} \mathbf{I}_2 \rightarrow \mathbf{I}_2$$

$$\mathbf{I}_2 = \frac{j\omega N_1 N_2 \mathcal{P}_{12}}{R_2 + j\omega N_2^2 \mathcal{P}_{12} g_2} \mathbf{I}_1 - \frac{\mathbf{V}_2}{R_2 + j\omega N_2^2 \mathcal{P}_{12} g_2} \Rightarrow \frac{N_2}{N_1} \mathbf{I}_2 = \frac{j\omega N_2^2 \mathcal{P}_{12}}{R_2 + j\omega N_2^2 \mathcal{P}_{12} g_2} \mathbf{I}_1 - \frac{\frac{N_2}{N_1} \mathbf{V}_2}{R_2 + j\omega N_2^2 \mathcal{P}_{12} g_2} \rightarrow \mathbf{I}_1$$

Also need  $\left| \frac{\mathbf{V}_1}{R_1 + j\omega L_1} \right| \ll |\mathbf{I}_1|$  and  $\left| \frac{\mathbf{V}_2}{R_2 + j\omega L_2} \right| \ll |\mathbf{I}_2|$ , so currents are due to coupling (only).

What is needed in transformer construction to achieve these limits?

**Problem 9.79: Find  $Z_{ab}$ , then repeat with the dot on one coil reversed.**

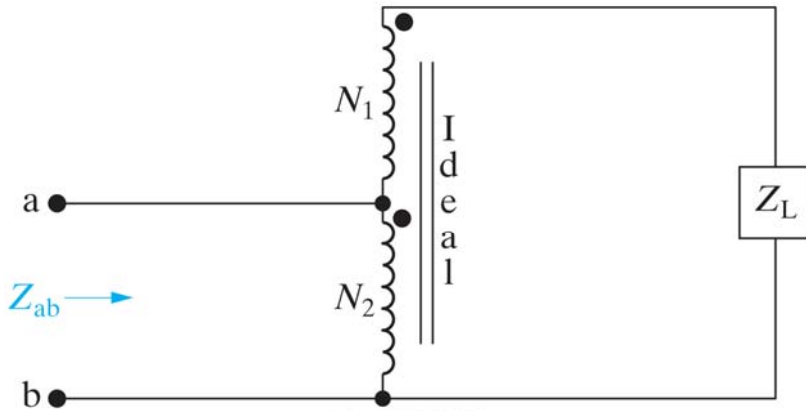


Figure: 09-58-56P9.79

Copyright © 2008 Pearson Prentice Hall, Inc.