

Laboratory 3: More Transformers

Objective: We will experiment again with the transformers from [Lab 2](#) and use the formulas for [linear](#) and [ideal](#) transformers, including the notes on [limits of the linear transformer equations](#) when the ideal transformer assumptions are applied.

Lab Activities:

1. Use the outer terminals on the secondary so that the turns ratio is expected to be $a=N_2 / N_1 = 0.1$.
2. Use a frequency of 100 Hz and characterize your transformer at this frequency. That is, estimate the internal resistances of the primary and secondary coils (R_1 and R_2), the self-inductances (L_1 and L_2), and the coefficient of coupling, k . You should be able to estimate R_1 , R_2 , L_1 , and L_2 quickly using the procedure from [Lab 2](#).
3. Compare the ratio L_1 / L_2 with the expected value of $[N_1 / N_2]^2 = 100$.
4. Determine how closely your transformer approximates the ideal transformer equations:
$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$
$$N_1 \mathbf{I}_1 = N_2 \mathbf{I}_2$$
$$Z_{ab} = \frac{Z_L}{(N_2/N_1)^2}$$
How does the closeness of approximation vary with frequency?
5. If you finish the previous steps, set up the circuit shown in Problem 9.82 that you analyzed on [Homework 3](#), and compare your measured results with the analysis. Use a potentiometer for R_x .

Each lab group should prepare a one-page summary of your results and discuss it with the instructor before leaving.

Please keep your circuits assembled until you discuss the results with the instructor.