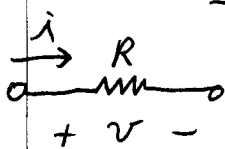


# Review of Chapter 6




$$v = i \cdot R$$

$$i = \frac{1}{R} v$$

$$p = v \cdot i = i^2 R = \frac{1}{R} v^2$$

$$w(t) = \int_{t_0}^t p(x) dx$$

= Energy dissipated during  $[t_0, t]$

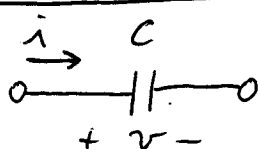


$$v(t) = \frac{1}{C} \int_{t_0}^t i(x) dx + v(t_0)$$

$$i = C \frac{dv}{dt}$$

$$p = v \cdot i$$

$$w(t) = \frac{1}{2} C v(t)^2$$

Energy stored at any time  $t$ .

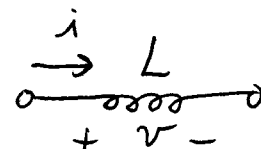

$$v = L \frac{di}{dt}$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v(x) dx + i(t_0)$$

$$w(t) = \frac{1}{2} L i(t)^2$$

Energy stored at any time  $t$ .

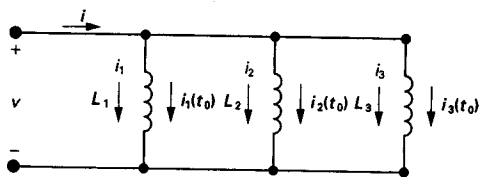


Figure 6.15 Three inductors in parallel.

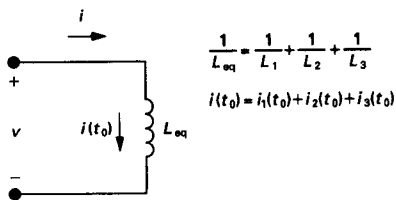


Figure 6.16 An equivalent circuit for three inductors in parallel.

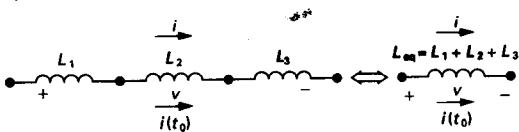


Figure 6.14 An equivalent circuit for inductors in series carrying an initial current  $i(t_0)$ .

