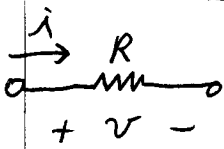


Review of Chapter 6 5




$$v = i \cdot R$$

$$i = \frac{1}{R} v$$

$$p = v \cdot i = i^2 R = \frac{1}{R} v^2$$

$$w(t) = \int_{t_0}^t p(x) dx$$

= Energy dissipated during $[t_0, t]$

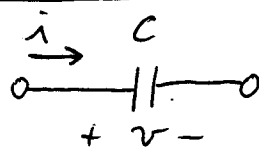


$$v(t) = \frac{1}{C} \int_{t_0}^t i(x) dx + v(t_0)$$

$$i = C \frac{dv}{dt}$$

$$p = v \cdot i$$

$$w(t) = \frac{1}{2} C v(t)^2$$

Energy stored at any time t .

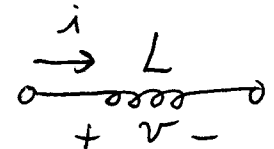

$$v = L \frac{di}{dt}$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v(x) dx + i(t_0)$$

$$w(t) = \frac{1}{2} L i(t)^2$$

Energy stored at any time t .

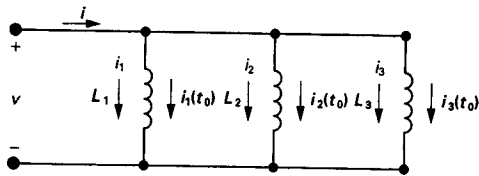


Figure 6.15 Three inductors in parallel.

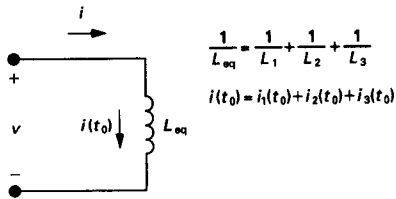


Figure 6.16 An equivalent circuit for three inductors in parallel.

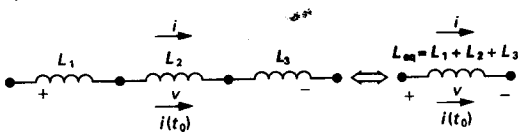


Figure 6.14 An equivalent circuit for inductors in series carrying an initial current $i(t_0)$.

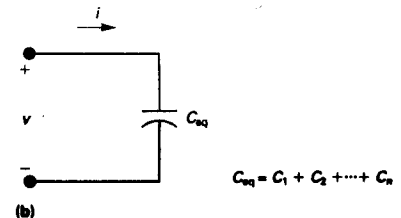
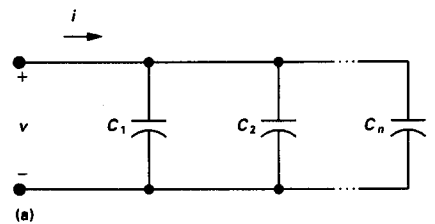
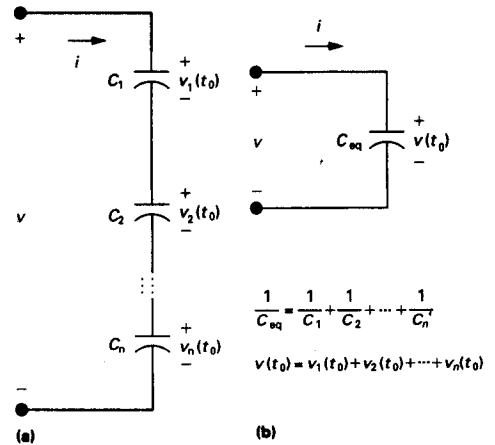


Table 5-4: Basic properties of R , L , and C .

Property	R	L	C
i - v relation	$i = \frac{v}{R}$	$i = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$	$i = C \frac{dv}{dt}$
v - i relation	$v = iR$	$v = L \frac{di}{dt}$	$v = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$
p (power transfer in)	$p = i^2 R$	$p = Li \frac{di}{dt}$	$p = Cv \frac{dv}{dt}$
w (stored energy)	0	$w = \frac{1}{2} Li^2$	$w = \frac{1}{2} Cv^2$
Series combination	$R_{eq} = R_1 + R_2$	$L_{eq} = L_1 + L_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$
Parallel combination	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$	$C_{eq} = C_1 + C_2$
dc behavior	no change	short circuit	open circuit
Can v change instantaneously?	yes	yes	no
Can i change instantaneously?	yes	no	yes