

LAB 4 DATA

Data is provided here for the transformer in Lab 4 that you may use for your report. The plots on pages 2-3 show traces that would be observed on the oscilloscope. Phases are stated with respect to $v_T(t)$, the voltage at the terminals of the waveform generator. The phasor voltages are *peak* values (not rms).

1. Source at primary with “helper” resistor $R_h = 10 \Omega$, open-circuit secondary:

$$\mathbf{V}_T = 0.54 \angle 0^\circ \text{ V}$$

$$\mathbf{V}_1 = 0.40 \angle 36.6^\circ \text{ V} .$$

$$\mathbf{V}_2 = 3.63 \angle 41.2^\circ \text{ V}$$

2. Source at secondary with “helper” resistor $R_h = 1 \text{ k}\Omega$, open-circuit primary:

$$\mathbf{V}_T = 19.61 \angle 0^\circ \text{ V}$$

$$\mathbf{V}_1 = 1.33 \angle 41.2^\circ \text{ V} .$$

$$\mathbf{V}_2 = 14.80 \angle 36.6^\circ \text{ V}$$

(When you calculate M , you can *average* the estimates obtained in parts 1 and 2. Ideally both would give the same result, but they are different due to measurement errors.)

3. Source at primary with “helper” resistor $R_h = 10 \Omega$, load resistor $R_L = 5 \text{ k}\Omega$ at secondary:

$$\mathbf{V}_T = 0.56 \angle 0^\circ \text{ V}$$

$$\mathbf{V}_1 = 0.39 \angle 32.4^\circ \text{ V} .$$

$$\mathbf{V}_2 = 3.34 \angle 34.3^\circ \text{ V}$$

Calculate the currents \mathbf{I}_1 and \mathbf{I}_2 from the voltage phasors, and compare the phasor voltages and currents with the ideal transformer equations using $n = \sqrt{L_2/L_1}$. How closely do the voltages and currents match the ideal transformer model?

Replace the transformer and load with a single “reflected impedance” \mathbf{Z}_R calculated using the linear and ideal transformer models (you will get a different \mathbf{Z}_R for each model). Which \mathbf{Z}_R gives a closer approximation to the given \mathbf{V}_1 and \mathbf{I}_1 phasor values?

Also calculate the average power delivered to the load resistor (using \mathbf{V}_2).

When the same load is attached at nodes $a-b$ with the same helper resistor:

$$\mathbf{V}_L = \mathbf{V}_{a-b} = 1.98 \angle 0^\circ \text{ V} .$$

Use this to calculate the average power delivered to load if the transformer is *removed*.

See plots of voltage waveforms on pages 2 and 3 (available online, but not included on handout given in class).



