

## Natural and Step Responses for RLC Circuits

The natural and step responses of RLC circuits are described by second-order, linear differential equations with constant coefficients and constant “input” (or forcing function),

$$a \frac{d^2 x}{dt^2} + b \frac{dx}{dt} + c x(t) = D, \quad (1)$$

where  $a, b, c$ , and  $D$  are constants, and the initial values  $x(0^+)$  and  $\frac{dx(0^+)}{dt}$  are known (these are found by circuit analysis). We assume  $a > 0$ , without loss of generality.

As you know from MATH 212, the general solution for  $t > 0$  is

$$x(t) = x_c(t) + x_p(t), \quad (2)$$

where  $x_c(t)$  is the complementary solution to the homogeneous equation and  $x_p(t)$  is a particular solution. The particular solution is

$$x_p(t) = \begin{cases} \frac{D}{c}, & c \neq 0 \\ \frac{D}{b}t, & c = 0, b \neq 0 \\ \frac{D}{2a}t^2, & c = b = 0 \end{cases} . \quad (3)$$

The homogeneous differential equation is

$$a \frac{d^2 x_c}{dt^2} + b \frac{dx_c}{dt} + c x_c(t) = 0. \quad (4)$$

Its solution is determined by the characteristic (or auxiliary) equation,

$$as^2 + bs + c = 0, \quad (5)$$

which has roots

$$s_1 = -\frac{b}{2a} + \sqrt{\left(\frac{b}{2a}\right)^2 - \frac{c}{a}} = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad (6)$$

$$s_2 = -\frac{b}{2a} - \sqrt{\left(\frac{b}{2a}\right)^2 - \frac{c}{a}} = -\alpha - \sqrt{\alpha^2 - \omega_0^2}. \quad (7)$$

The neper frequency is  $\alpha = b/(2a)$  and the resonant frequency is  $\omega_0 = \sqrt{c/a}$  (in radians/sec). If  $c < 0$ , then  $\omega_0$  is imaginary and  $s_1 > 0$  in (6).

There are three cases.

1. Real and unequal roots (overdamped):  $\alpha^2 > \omega_0^2$

$$x_c(t) = c_1 e^{s_1 t} + c_2 e^{s_2 t} \quad (8)$$

Both terms are *decaying* exponentials if  $c > 0$ .

2. Real and equal roots (critically damped):  $\alpha^2 = \omega_0^2$

$$x_c(t) = c_1 e^{s_1 t} + c_2 t e^{s_1 t}, \quad \text{where } s_1 = -\alpha = -\frac{b}{2a} \quad (9)$$

3. Complex roots (underdamped):  $\alpha^2 < \omega_0^2$

The roots have the form

$$s_{1,2} = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2} = -\alpha \pm j\omega_d \quad (10)$$

where  $\omega_d$  is the damped frequency (in radians/sec). Then

$$x_c(t) = c_1 e^{-\alpha t} \cos(\omega_d t) + c_2 e^{-\alpha t} \sin(\omega_d t) \quad (11)$$

In the case that  $\alpha = 0$ , then  $\omega_d = \omega_0$  and the solution is pure, undamped oscillation,

$$x_c(t) = c_1 \cos(\omega_0 t) + c_2 \sin(\omega_0 t). \quad (12)$$

This is why  $\omega_0$  is called the *resonant frequency*.

Summary:

- The general solution is in equation (2):  $x(t) = x_c(t) + x_p(t)$ .
- The complementary solution  $x_c(t)$  is either (8), (9), or (11).
- The particular solution  $x_p(t)$  is in (3). For the natural response,  $D = 0$  and  $x_p(t) = 0$ .
- The constants  $c_1$  and  $c_2$  are determined from the initial conditions  $x(0^+)$  and  $\frac{dx(0^+)}{dt}$ .
- Hints for finding initial conditions in RLC circuits:
  - Parallel RLC: Analyze voltages, so  $x(t) = v(t)$ . Then  $v(0^+)$  is determined from the initial capacitor voltage, and  $\frac{dv(0^+)}{dt}$  is determined from KCL and the initial inductor current.
  - Series RLC: Analyze currents, so  $x(t) = i(t)$ . Then  $i(0^+)$  is determined from the initial inductor current, and  $\frac{di(0^+)}{dt}$  is determined from KVL and the initial capacitor voltage.